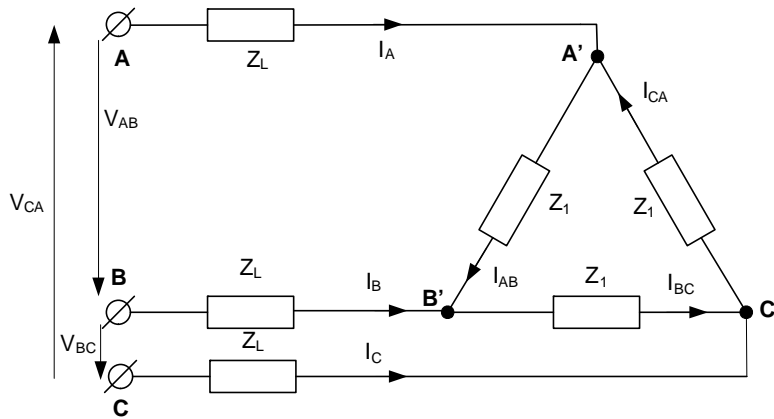


TUTORIAL 7: THREE-PHASE POWER SYSTEMS

7.1: Three $(30 + j30) \Omega$ identical impedances are connected in Delta and supplied by a 173V 3-phase system through three lines each having impedance of $(0.8 + j0.6) \Omega$. Find:


- 1) the current magnitude in each of the delta-connected impedances, and
- 2) the voltage across each of Delta impedance.

Solution: (Single phase calculation for a three phase balanced system)



$$\text{KCL: } I_A + I_{CA} - I_{AB} = 0$$



$$I_A = I_{AB} - I_{CA}$$

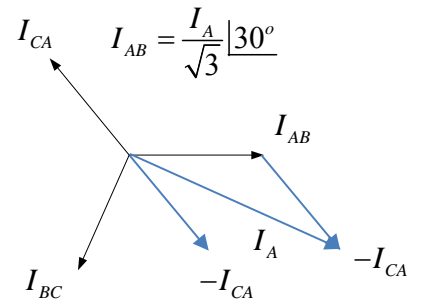

For single phase calculation both Δ loads and sources have to be connected into Y.

Convert Δ loads into Y: $Z_{Load} = Z_1 / 3 = (10 + j10) \Omega$

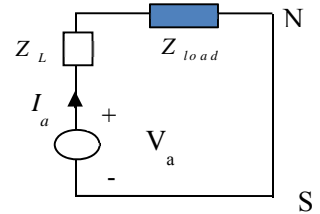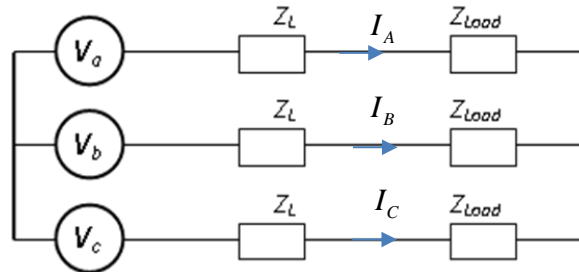Y sources phase voltages: $V_a = \frac{173V}{\sqrt{3}} \angle 0^\circ$; $V_b = \frac{173V}{\sqrt{3}} \angle -120^\circ$; $V_c = \frac{173V}{\sqrt{3}} \angle -240^\circ$



The total (per phase) impedance: $Z_T = Z_L + Z_{Load} = 10.8 + j10.6 = 15.133 \angle 44.46^\circ \Omega$

The phase currents: $I_A = \frac{V_a}{Z_T} = 6.60 \angle -44.46^\circ (A)$; $I_B = I_A \angle -120^\circ$; $I_C = I_A \angle -240^\circ$

The current in each of the delta load:

$$I_{AB} = \frac{I_A}{\sqrt{3}} \angle +30^\circ; \quad I_{BC} = I_{AB} \angle -120^\circ; \quad I_{CA} = I_{AB} \angle -240^\circ$$

The voltages of the delta connected load:

$$V_{A'B'} = I_{AB} Z_1 = 161.64 \angle 30.54^\circ (V); \quad V_{B'C'} = V_{A'B'} \angle -120^\circ (V); \quad V_{C'A'} = V_{A'B'} \angle -240^\circ (V)$$

7.2: A 415V, 50 HZ, 4-wire three-phase balanced power supply with sequence RYB is connected to the following loads:

A single resistance of $12\ \Omega$ between R phase and neutral;

An inductive impedance of $(2 + j8)\ \Omega$ between B phase and neutral;


A capacitor of $120\ \mu\text{F}$ between R and Y phase;

A three-phase, delta connected induction motor operating at 10kW and 0.75 p.f. lagging.

Calculate:

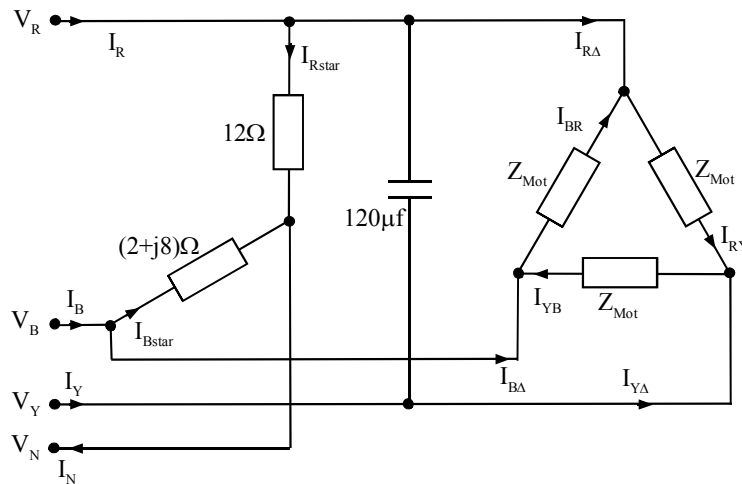- 1) the magnitude and phase angle of the current in the four lines of the supply, and
- 2) the total power from the supply.

Solutions: (unbalanced three phase system)



The phase supply voltages (**using phase R voltage as the reference**):

$$V_R = \frac{415V}{\sqrt{3}} \angle 0^\circ$$

$$V_Y = \frac{415V}{\sqrt{3}} \angle -120^\circ$$

$$V_B = \frac{415V}{\sqrt{3}} \angle -240^\circ$$

The line to line supply voltages:

$$V_{RY} = 415V \angle 30^\circ$$

$$V_{YB} = 415V \angle -90^\circ$$

$$V_{BR} = 415V \angle -210^\circ$$

The current in $12\ \Omega$ load :

$$I_{R_star} = \frac{V_{RN}}{R} = \frac{415 \angle 0^\circ}{\sqrt{3}12} = 19.9667\ \text{A} \angle 0^\circ$$

The current in the $(2 + j8)\ \Omega$ inductor:

$$I_{B_star} = \frac{V_{BN}}{Z} = \frac{415 \angle -240^\circ}{\sqrt{3}(2 + j8)} = 29.0558\ \text{A} \angle 44.0362^\circ$$

The current in the 120μF capacitor:

$$I_{RY_cap} = \frac{V_{RY}}{Z_c} = \frac{415\angle 30^\circ}{1/j(2\pi 50)(120\mu f)} = 15.6451 A\angle 120^\circ$$

The inductive motor load 10kW, 0.75pf lagging: **(phase current lags phase voltage)**

The power factor angle: $\phi = \cos^{-1}(0.75) = 41.41^\circ$

The reactive power: $Q = P \tan \phi = 10,000 \tan(41.41^\circ) = 8.8192 kVar$

Since: $S = P + jQ = 3V_p I_p^*$

The terminal currents of the motor load:

$$I_{R_A} = \left(\frac{S}{3V_p} \right)^* = \left(\frac{10,000 + j8819.2}{\sqrt{3} \times 415\angle 0^\circ} \right)^* = 18.55 A\angle -41.41^\circ$$

$$I_{Y_A} = 18.55 A\angle -161.41^\circ$$

$$I_{B_A} = 18.55 A\angle 78.59^\circ$$

The four supply line currents (**unbalance**):

$$I_R = I_{R_star} + I_{RY_cap} + I_{R_A} = 26.09 A\angle 2.82^\circ$$

$$I_Y = -I_{RY_cap} + I_{Y_A} = 21.77 A\angle -116.63^\circ$$

$$I_B = I_{B_star} + I_{B_A} = 45.56 A\angle 57.39^\circ$$

$$I_N = I_{R_star} + I_{B_star} = 45.57 A\angle 26.31^\circ$$


The total power taken from the supply (**unbalance**):

$$S = V_R I_R^* + V_Y I_Y^* + V_B I_B^* = 16.473 kW + j 9.080 kVar$$

7.3: The figure below shows the per-phase per-unit network of a 4-bus power system.

Develop Thevenin equivalent circuits as viewed

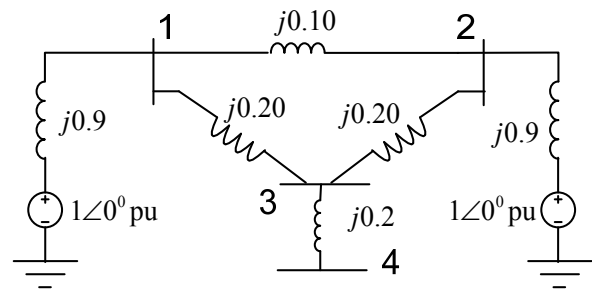- 1) from bus 4 and ground, and
- 2) from bus 2 and ground.




Solutions:

1) From bus 4 and ground:

Equivalent network of the original circuit using delta-Y transform:

$$Z_a = \frac{Z_{ab}Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}} = \frac{j0.20 \times j0.20}{j0.20 + j0.20 + j0.10} = j0.08$$
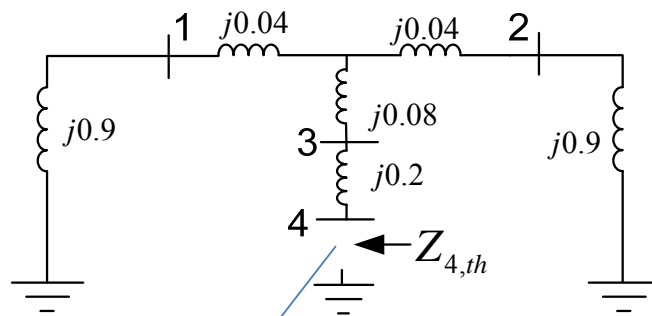
$$Z_b = Z_c = \frac{Z_{ab}Z_{bc}}{Z_{ab} + Z_{bc} + Z_{ca}} = \frac{j0.20 \times j0.10}{j0.20 + j0.20 + j0.10} = j0.04$$



Thevenin impedance (kill all the sources in the original circuit):


$$Z_{4,th} = j0.28 + (j0.04 + j0.9) \parallel (j0.04 + j0.9) = j0.75$$

$$?? Z_{4,th} = j0.2 + (j0.2 + j0.9) \parallel (j0.2 + j0.9) = j0.75$$


Thevenin Voltage (Open circuit voltage):

$$V_{4,th} = 1\angle 0^\circ$$

Thevenin equivalent circuit:

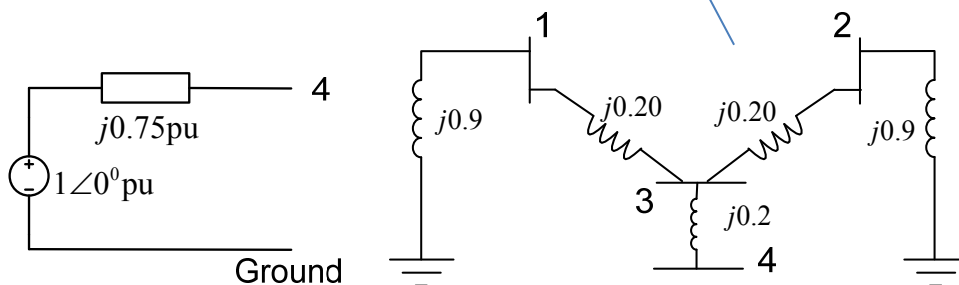

2) from bus 2 and ground:

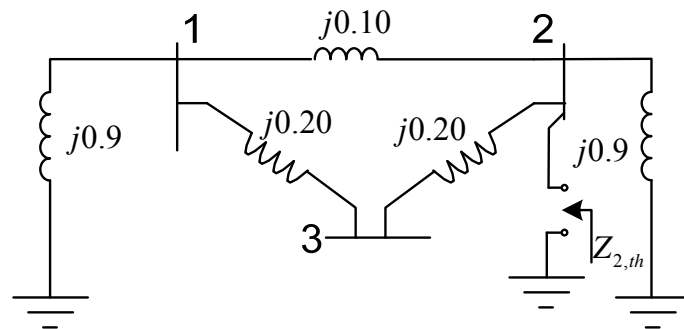

Thevenin impedance:

$$Z_{2,th} = j0.9 \parallel [(j0.2 + j0.2) \parallel j0.1 + j0.9] = j0.9 \parallel j0.98 = j0.4692 \text{ pu} = Z_{22}$$

Open-circuit voltage as viewed from bus 2:

$$V_{2,th} = 1 \angle 0^\circ \text{ pu}$$

Thevenin equivalent circuit:

