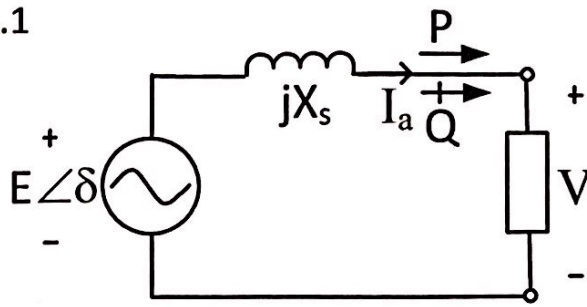


EE3015 Tutorial #4

4.1



$$S_b = 24 \text{ MVA}, V_b = 17.32 \text{ kV}$$

$$Z_b = 17.32^2 / 24 = 12.5 \Omega$$

$$X_s = 5 / 12.5 = 0.4 \text{ pu}$$

$$I_b = S_b / (\sqrt{3} \times V_b) = 0.8 \text{ kA}$$

(i) $V = 17.32 / V_b = 1 \angle 0^\circ \text{ pu}$; Ref angle

$$S = \frac{\text{Rated MVA}}{S_b} \angle 36.87^\circ = \frac{24}{24} \angle 36.87^\circ = 1 \angle 36.87^\circ \text{ pu}$$

$$I_a = (S/V)^* = 1 \angle -36.87^\circ \text{ pu}$$

$$E = V + jX_s I_a = 1 \angle 0^\circ + 0.4 \angle 90^\circ \times 1 \angle -36.87^\circ = 1.2806 \angle 14.47^\circ \text{ pu}$$

$$\text{Internal emf per phase} = |E_p| = 1.2806 \times V_b / \sqrt{3} = 12.806 \text{ kV}$$

$$\text{Power angle of the generator} = \delta = 14.47^\circ$$

(ii) $|E| = 13.4 \times \sqrt{3} / V_b = 1.34 \text{ pu}$, $|V| = 10 \times \sqrt{3} / V_b = 1 \text{ pu}$

$$P_{\max} = \frac{EV}{X_s} \sin \delta \Big|_{\delta=90^\circ} = \frac{1.34 \times 1}{0.4} = 3.35 \text{ pu}$$

$$\text{Actual } P_{\max} = 3.35 \times 24 = 80.4 \text{ MW}$$

$$Q \text{ at } P_{\max} \text{ or } Q = \frac{V}{X_s} (E \cos \delta - V) \Big|_{\delta=90^\circ} = -\frac{V^2}{X_s} = -\frac{1}{0.4} = -2.5 \text{ pu}$$

Actual $Q = -2.5 \times 24 = -60 \text{ Mvar}$ or 60 Mvar absorbed by the generator

$$S = 3.35 - j2.5 = 4.18 \angle -36.73^\circ \text{ pu}$$


$$I_a = \left(\frac{S}{V} \right)^* = \left(\frac{4.18 \angle -36.73^\circ}{1 \angle 0^\circ} \right)^* = 4.18 \angle 36.73^\circ \text{ pu}$$

$$\text{Actual } |I_a| = 4.18 \times I_b = 4.18 \times 0.8 = 3.344 \text{ kA}$$

Alternative approach: When $\delta = 90^\circ$, E is perpendicular to V .

Using Pythagoras' theorem for a right-angled triangle:
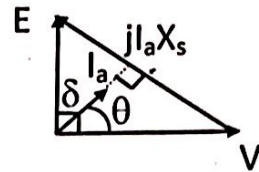
$$I_a X_s = \sqrt{E^2 + V^2} = \sqrt{1.34^2 + 1^2} = 1.672 \text{ pu}$$



$$I_a = 1.672 / 0.4 = 4.18 \text{ pu}$$

$$4.2 \quad P_{f1} = P_{f2} = 3 \text{ MW}, f_{f1} = f_{f2} = 49 \text{ Hz}, f_{n1} = 52 \text{ Hz and } f_{n2} = 51 \text{ Hz}$$

$$S_{p1} = \frac{P_{f1}}{f_{n1} - f_{f1}} = \frac{3}{52 - 49} = 1 \text{ MW/Hz}$$

$$S_{p2} = \frac{P_{f2}}{f_{n2} - f_{f2}} = \frac{3}{51 - 49} = 1.5 \text{ MW/Hz}$$

$$P_{G1} = S_{p1} (f_{n1} - f_{sys})$$

$$P_{G2} = S_{p2} (f_{n2} - f_{sys})$$

$$(a) \quad P_{\text{Load}} = P_{G1} + P_{G2} \rightarrow 4 = 1(52 - f_{sys}) + 1.5(51 - f_{sys})$$

$$f_{sys} = (128.5 - 4) / 2.5 = 49.8 \text{ Hz}$$

$$P_{G1} = 1(52 - f_{sys}) = 52 - 49.8 = 2.2 \text{ MW}$$

$$P_{G2} = 1(51 - f_{sys}) = 51 - 49.8 = 1.8 \text{ MW}$$

$$(b) S_{\text{Load}} = \frac{P_{\text{Load}}}{\text{pf}_{\text{Load}}} \angle \cos^{-1} 0.8 = \frac{4}{0.8} \angle 36.87^\circ = 5 \angle 36.87^\circ \text{ MVA}$$

$$S_{G1} = \frac{P_{G1}}{\text{pf}_{G1}} \angle \cos^{-1} 0.85 = \frac{2.2}{0.85} \angle 31.788^\circ = 2.588 \angle 31.788^\circ \text{ MVA}$$

$$S_{\text{Load}} = S_{G1} + S_{G2} \rightarrow S_{G2} = S_{\text{Load}} - S_{G1} = 5 \angle 36.87^\circ - 2.588 \angle 31.788^\circ$$

$$S_{G2} = 2.433 \angle 42.28^\circ$$

Power factor of Generator #2 = $\cos 42.28^\circ = 0.74$ lag (lag because S_{G2} has a positive angle)

(c) $f_{n/2} = ?$ to bring the system frequency back to 50 Hz


$$P'_{G1} = S_{p1} (f'_{n/1} - f'_{\text{sys}}) = 1(52 - 50) = 2 \text{ MW}$$

$$P'_{G2} = P_{\text{Load}} - P'_{G1} = 4 - 2 = 2 \text{ MW}$$

$$2 = P'_{G2} = S_{p2} (f'_{n/2} - f'_{\text{sys}}) = 1.5 (f'_{n/2} - 50) = 1.5 f'_{n/2} - 75$$

$$f'_{n/2} = (75 + 2)/1.5 = 77/1.5 = 51.33 \text{ Hz}$$

Power-Frequency diagram:

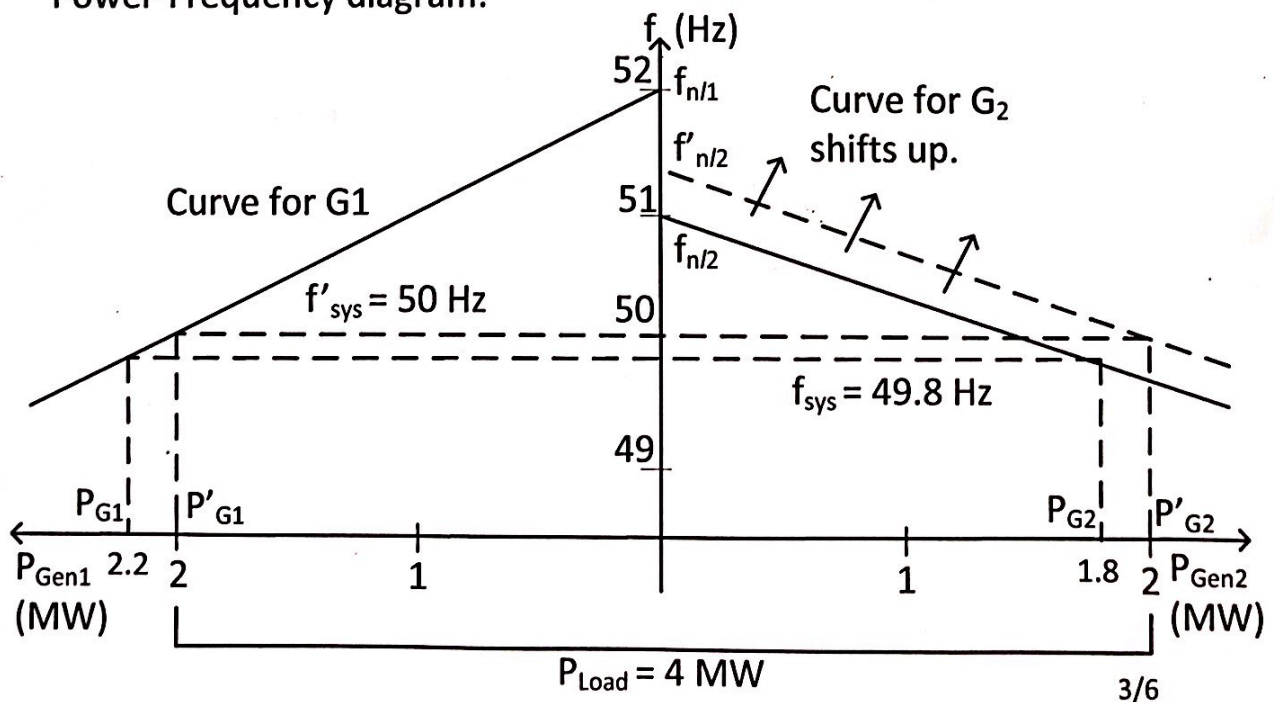

$$4.3 \quad n = \frac{120f}{p} \rightarrow f_{nl} = \frac{n_{nl} \times p}{120} \text{ and } f_{fl} = \frac{n_{fl} \times p}{120}$$

$$f_{nl1} = \frac{n_{nl1} \times p_1}{120} = \frac{3040 \times 2}{120} = 50.67 \text{ Hz}$$

$$f_{fl1} = \frac{n_{fl1} \times p_1}{120} = \frac{2975 \times 2}{120} = 49.58 \text{ Hz}$$

$$f_{nl2} = \frac{n_{nl2} \times p_2}{120} = \frac{1500 \times 4}{120} = 50 \text{ Hz}$$

$$f_{fl2} = \frac{n_{fl2} \times p_2}{120} = \frac{1485 \times 4}{120} = 49.5 \text{ Hz}$$

$$(a) \quad S_{p1} = \frac{P_{fl1}}{f_{nl1} - f_{fl1}} = \frac{200}{50.67 - 49.58} = 185 \text{ kW / Hz}$$

$$S_{p2} = \frac{P_{fl2}}{f_{nl2} - f_{fl2}} = \frac{150}{50 - 49.5} = 300 \text{ kW / Hz}$$

$$P_{Load} = P_{G1} + P_{G2} = S_{p1} (f_{nl1} - f_{sys}) + S_{p2} (f_{nl2} - f_{sys})$$

$$200 = 185(50.67 - f_{sys}) + 300(50 - f_{sys})$$

$$f_{sys} = (24,373.95 - 200)/485 = 49.843 \text{ Hz}$$

$$(b) \quad P_{G1} = S_{p1} (f_{nl1} - f_{sys}) = 185(50 - 49.843) = 153 \text{ kW}$$

$$P_{G2} = P_{Load} - P_{G1} = 200 - 153 = 47 \text{ kW}$$


$$4.4 \quad S_b = 3/0.8 = 3.75 \text{ MVA}, V_b = 6.6 \text{ kV} \rightarrow Z_b = 6.6^2/3.75 = 11.616 \Omega$$

$$I_b = S_b/(\sqrt{3} V_b) = 3.75/(\sqrt{3} \times 6.6) = 0.328 \text{ kA}$$

$$V = 6.6 / V_b = 1 \angle 0^\circ \text{ pu, Ref}$$

$$S_L = \frac{3/0.8}{S_b} \angle \cos^{-1} 0.8$$
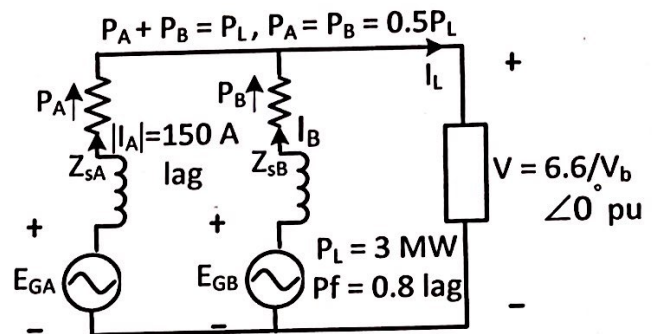
$$= \frac{3.75}{3.75} \angle 36.87^\circ = 1 \angle 36.87^\circ \text{ pu}$$



$$I_L = \left(\frac{S_L}{V} \right)^* = \left(\frac{1 \angle 36.87^\circ}{1 \angle 0^\circ} \right)^* = 1 \angle -36.87^\circ \text{ pu}$$

$$Z_{sA} = \frac{0.5 + j10}{11.616} = 0.862 \angle 87.138^\circ \text{ pu}$$

$$Z_{sB} = \frac{0.4 + j12}{11.616} = 1.034 \angle 88.091^\circ \text{ pu}$$

$$I_A = 150 \text{ A lag (Given)}$$

$$\text{Magnitude of } I_A = 150/328 = 0.4753 \text{ pu}$$

Phasor angle of I_A is solved as follows:

$$P_A = P_B = \frac{0.5 P_L}{S_b} = \frac{1.5}{3.75} = 0.4 \text{ pu}$$

$$P_A = |V| |I_A| \cos \theta_A = 0.4 \rightarrow \cos \theta_A = P_A / (|V| |I_A|) = 0.4 / 0.4753 = 0.8747 \text{ lag}$$

Note that lag is given by the problem and is not computed.

$$\theta_A = \cos^{-1} 0.8747 = 29^\circ \text{ lag} \rightarrow I_A = 0.4573 \angle -29^\circ \text{ pu}$$

$$I_B = I_L - I_A = 1 \angle -36.87^\circ - 0.4573 \angle -29^\circ = 0.5506 \angle -43.41^\circ \text{ pu}$$

$$\text{Actual } |I_B| = 0.5506 \times I_b = 0.5506 \times 328 = 180.63 \text{ A}$$

Power factor of Gen B = $\cos 43.41^\circ = 0.7264$ lag; lag because the phasor angle of I_B is negative with respect to that of the V phasor.

$$E_{GA} = V + Z_{sA} I_A = 1 \angle 0^\circ + 0.862 \angle 87.138^\circ \times 0.4573 \angle -29^\circ = 1.2536 \angle 15.49^\circ \text{ pu}$$

$$\text{Actual } |E_{GA}| = 1.2536 \times V_b = 1.2536 \times 6.6 = 8.274 \text{ kV}; \delta_A = 15.49^\circ$$

$$E_{GB} = V + Z_{sB} I_B = 1 \angle 0^\circ + 1.034 \angle 88.091^\circ \times 0.5506 \angle -43.41^\circ = 1.4605 \angle 15.9^\circ \text{ pu}$$

$$\text{Actual } |E_{GB}| = 1.4605 \times V_b = 1.4605 \times 6.6 = 9.640 \text{ kV}; \delta_B = 15.9^\circ$$

Phasor diagram:

