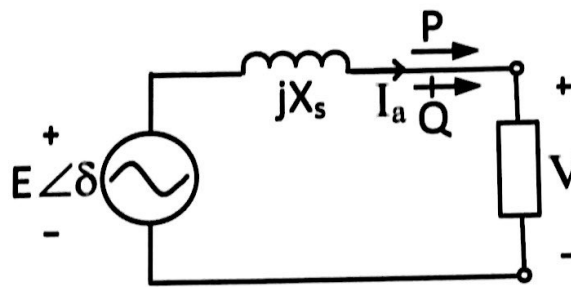


EE3015 Tutorial #3

3.1



$$S_b = 125 \text{ MVA}, V_b = 13.2 \text{ kV}$$

$$Z_b = 13.2^2 / 125 = 1.3939 \Omega$$

$$X_s = 1.7 / 1.3939 = 1.2196 \text{ pu}$$

$$(a) V = 13.2 / V_b = 1 \angle 0^\circ \text{ pu; Ref}$$

$$S = \frac{100}{125} \angle 0^\circ = 0.8 \angle 0^\circ \text{ pu}$$

$$I_{a1} = (S/V)^* = 0.8 \angle 0^\circ \text{ pu}$$

$$E_1 = V + jX_s I_{a1} = 1 \angle 0^\circ + 1.2196 \angle 90^\circ \times 0.8 \angle 0^\circ = 1.3971 \angle 44.295^\circ \text{ pu}$$

$$|E_1| = 1.3971 \times V_b = 1.3971 \times 13.2 = 18.442 \text{ kV}; \delta_1 = 44.295^\circ$$

$Q_1 = 0$ due to unity pf.

(b) We assume that the generator has zero internal loss. Hence if the prime mover input to the generator is reduced by 50%:

$$P_2 = P_1 / 2 = 100 / 2 = 50 \text{ MW} \rightarrow P_2 = 50 / S_b = 50 / 125 = 0.4 \text{ pu}$$

Without changing the excitation $\rightarrow |E_2| = |E_1|$ in part (a)

$$P_2 = \frac{E_2 V}{X_s} \sin \delta_2 \rightarrow 0.4 = \frac{1.3971 \times 1}{1.2196} \sin \delta_2$$

$$\delta_2 = \sin^{-1} \frac{0.4 \times 1.2196}{1.3971} = 20.437^\circ; |E_2| \text{ remains the same as before.}$$

$$Q_2 = \frac{V}{X_s} (E_2 \cos \delta_2 - V) = \frac{1}{1.2196} (1.3971 \cos 20.437^\circ - 1) = 0.2535 \text{ pu}$$

$$Q_2 = 0.2535 \times S_b = 0.2535 \times 125 = 31.687 \text{ Mvar (produced by the generator)}$$

$$(c) P_3 = P_1 = 0.8 \text{ pu} = \text{Constant power} \rightarrow E \sin \delta = \text{Constant}$$

This means that $E_3 \sin \delta_3 = E_1 \sin \delta_1$. However, we know E_1 and δ_1 but not E_3 and δ_3 . Hence we are not able to solve E_3 and δ_3 .

Applying the other constant power equation: $I_{a3} \cos \theta_3 = I_{a1} \cos \theta_1$.
Therefore $I_{a3} \times 0.8 = 0.8 \times 1 \rightarrow I_{a3} = 1$ pu.

$I_{a3} = 1 \angle 36.87^\circ$ pu; positive for leading angle (first quadrant).


Alternative approach: Form S_3 from 100 MW, 0.8 pf leading and S_b .
Obtain I_{a3} from $I_{a3} = (S_3/V)^*$.

$$E_3 = V + jX_s I_{a3} = 1 \angle 0^\circ + 1.2196 \angle 90^\circ \times 1 \angle 36.87^\circ = 1.0119 \angle 74.63^\circ \text{ pu}$$


$$|E_3| = 1.0119 \times V_b = 1.0119 \times 13.2 = 13.357 \text{ kV}; \delta_3 = 74.63^\circ$$

$$Q_3 = -V I_{a3} \sin \theta_3 = -1 \times 1 \sin 36.87^\circ = -0.6 \text{ pu}$$

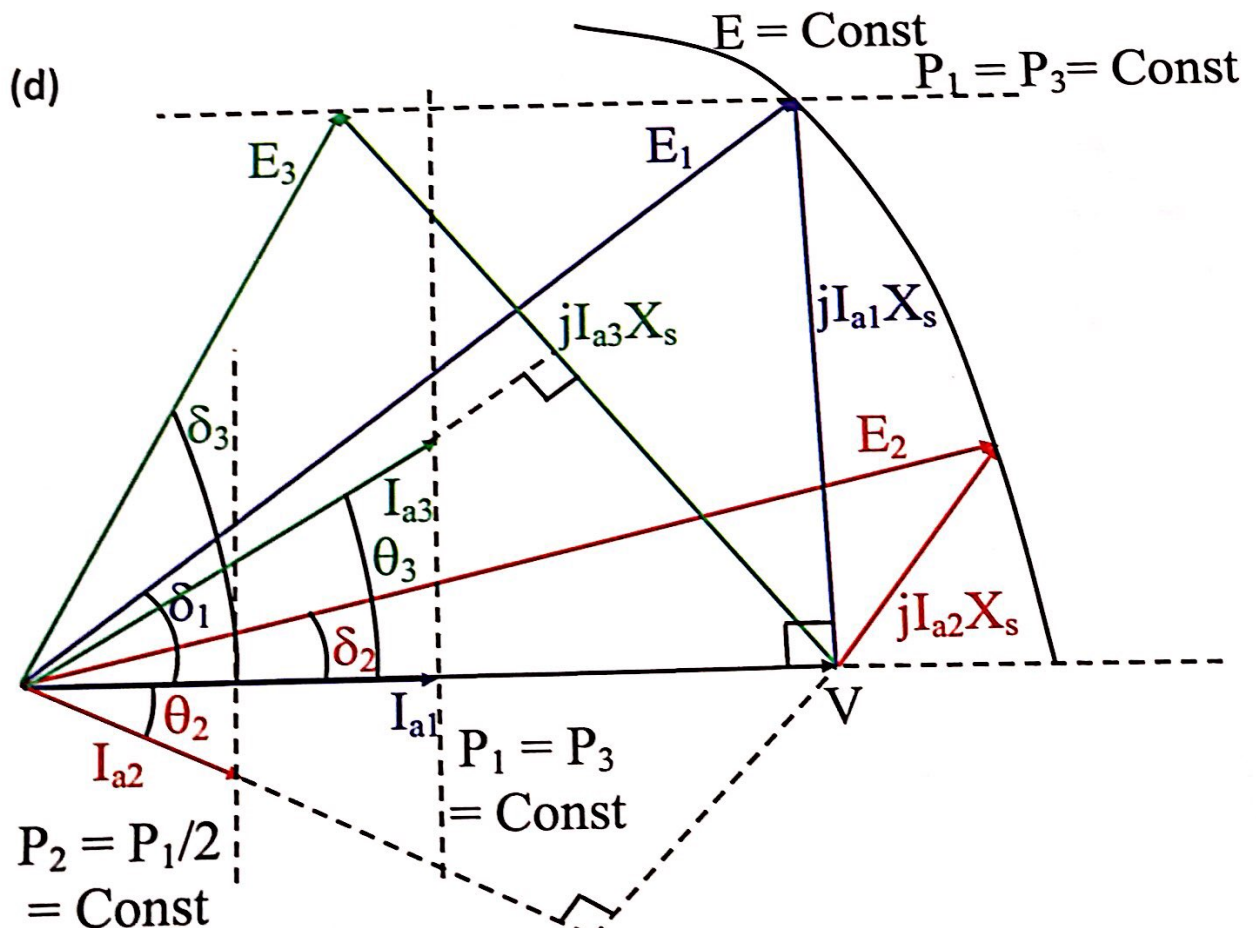Actual $Q_3 = -0.6 \times S_b = -75 \text{ Mvar}$ (or 75 Mvar absorbed by the generator).


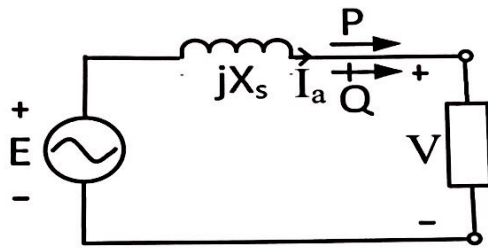
$$3.2 \quad I_b = 188 \text{ A}, V_b = 13.2 \text{ kV} \rightarrow S_b = \frac{\sqrt{3}V_b I_b}{1000} = 4.298 \text{ MVA}$$



$$Z_b = 13.2^2 / 4.298 = 40.537 \Omega$$

$$X_s = 10 / 40.537 = 0.2467 \text{ pu}$$

$$V = \frac{13.2}{V_b} = 1 \angle 0^\circ \text{ pu, ref angle} = 0^\circ$$

$$S_{old} = \frac{\sqrt{3} \times 13.2 \times 0.188}{S_b} = 1 \angle 0^\circ \text{ pu; } 0^\circ \text{ because of unity pf}$$

$$I_{a,old} = \left(\frac{S_{old}}{V} \right)^* = \left(\frac{1 \angle 0^\circ}{1 \angle 0^\circ} \right)^* = 1 \angle 0^\circ \text{ pu}$$

$$E_{old} = V + jX_s I_{a,old} = 1 \angle 0^\circ + 0.2467 \angle 90^\circ \times 1 \angle 0^\circ = 1.03 \angle 13.857^\circ \text{ pu}$$

$$|E_{new}| = 1.25 |E_{old}|$$

Without changing the mechanical power input $\rightarrow P = \text{Constant}$


$$E_{new} \sin \delta_{new} = E_{old} \sin \delta_{old} \rightarrow 1.25 E_{old} \sin \delta_{new} = E_{old} \sin \delta_{old}$$


$$\delta_{new} = \sin^{-1} (\sin 13.857^\circ / 1.25) = 11.046^\circ$$

$$I_{a,new} = \frac{E_{new} - V}{jX_s} = \left(\frac{1.25 \times 1.03 \angle 11.046^\circ - 1 \angle 0^\circ}{0.2467 \angle 90^\circ} \right) = 1.4636 \angle -46.9^\circ \text{ pu}$$

$$\text{Actual } |I_{a,new}| = 1.4636 \times I_b = 1.4636 \times 188 = 275.15 \text{ A}$$
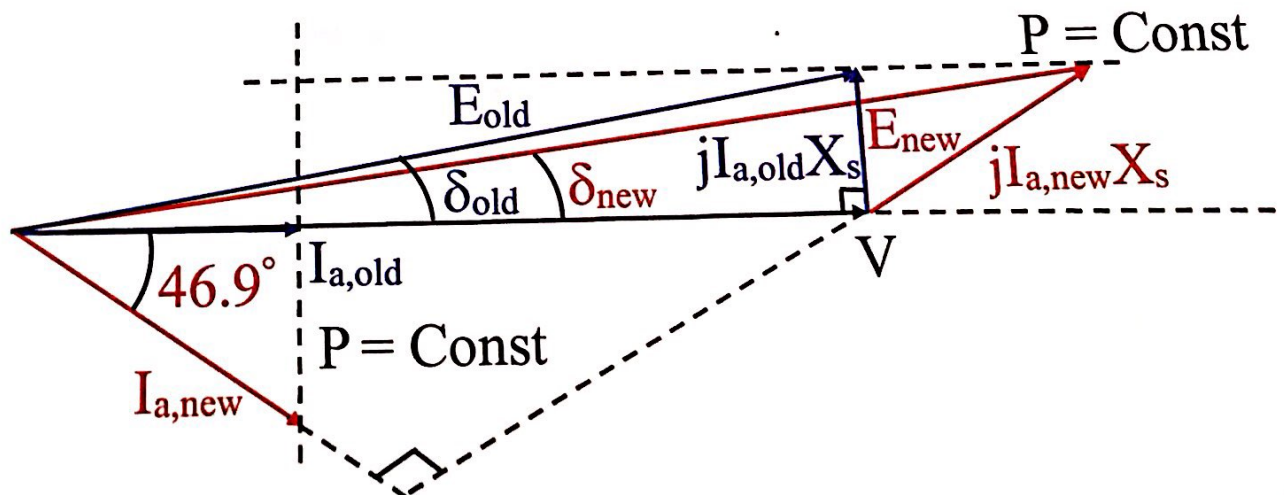
$$\text{pf of generator} = \cos 46.9^\circ = 0.683 \text{ lag } (I_{a,new} \text{ lags } V)$$



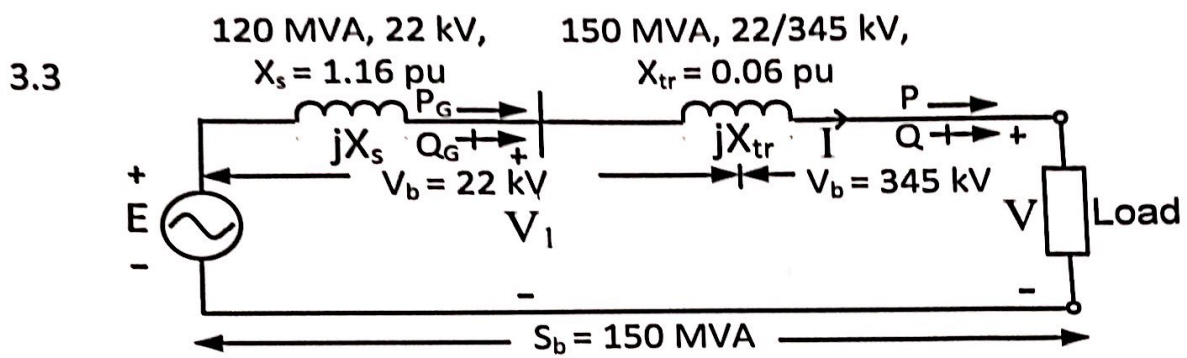

$$X_s = 1.16 \times \frac{150}{120} = 1.45 \text{ pu after converting to } S_b = 150 \text{ MVA}$$

(a) $V = 345/V_b = 345/345 = 1 \angle 0^\circ$ pu

$$S_{\text{Load}} = \left(\frac{80}{0.8} \angle -36.87^\circ \right) / 150 = 0.667 \angle -36.87^\circ \text{ pu}$$

$$I = \left(\frac{S_{\text{Load}}}{V} \right)^* = \left(\frac{0.667 \angle -36.87^\circ}{1 \angle 0^\circ} \right)^* = 0.667 \angle 36.87^\circ \text{ pu}$$

$$V_1 = V + jX_{tr} I = 1 \angle 0^\circ + 0.06 \angle 90^\circ \times 0.667 \angle 36.87^\circ = 0.9765 \angle 1.88^\circ \text{ pu}$$

$$\text{Actual } |V_1| = 0.9765 \times V_b = 0.9765 \times 22 = 21.4835 \text{ kV}$$

$$E = V_1 + jX_s I = 0.9765 \angle 1.88^\circ + 1.45 \angle 90^\circ \times 0.667 \angle 36.87^\circ = 0.8974 \angle 63.815^\circ \text{ pu}$$

$$\text{Actual } |E| = 0.8974 \times V_b = 0.8974 \times 22 = 19.743 \text{ kV}$$

(b) (i) $|E'| = 1.2|E|$ where $E = 0.8974 \angle 63.815^\circ$ from (a)

$$\text{Constant load of 80 MW} \rightarrow P = \text{Constant} \rightarrow E' \sin \delta' = E \sin \delta \rightarrow 1.2E \sin \delta' = E \sin 63.815^\circ$$

$$\delta' = \sin^{-1} (\sin 63.815^\circ / 1.2) = 48.4^\circ$$

$$I' = \frac{E' - V}{j(X_s + X_{tr})} = \left(\frac{1.2 \times 0.8974 \angle 48.4^\circ - 1 \angle 0^\circ}{1.51 \angle 90^\circ} \right) = 0.5657 \angle 19.49^\circ \text{ pu}$$

$$V_1' = V + jX_{tr} I' = 1 \angle 0^\circ + 0.06 \times 0.5657 \angle 109.49^\circ = 0.9892 \angle 1.854^\circ \text{ pu}$$

$$\text{Actual generator terminal voltage} = 0.9892 \times 22 = 21.762 \text{ kV}$$

$$(b) (ii) S_G = P_G + jQ_G = V_1' (I')^*$$

$$\begin{aligned} Q_G &= \text{Imag}[V_1' (I')^*] = \text{Imag}[0.9892 \angle 1.854^\circ \times 0.5657 \angle -19.49^\circ] \\ &= \text{Imag}[0.5596 \angle -17.64^\circ] = 0.5596 \times \sin(-17.64^\circ) = -0.1697 \text{ pu} \end{aligned}$$

$$\begin{aligned} \text{Actual reactive power output of the generator} &= -0.1697 \times 150 \\ &= -25.43 \text{ Mvar or } 25.43 \text{ Mvar absorbed by the generator} \end{aligned}$$

$$\text{Alternative approach: Use } Q_G = \frac{V_1'}{X_s} (E' \cos \delta' - V_1')$$

Note that you cannot substitute $\delta' = 48.4^\circ$ in the above equation since the ref angle of V_1' is NOT at zero degree. Instead you need to substitute $\delta' = 48.4^\circ - 1.854^\circ = 46.546^\circ$ since this is the angle difference between E' and V_1'

$$(b) (iii) S = P + jQ = V(I')^*$$

$$\begin{aligned} Q &= \text{Imag}[V(I')^*] = \text{Imag}[1 \angle 0^\circ \times 0.5657 \angle -19.49^\circ] \\ &= \text{Imag}[0.5657 \angle -19.49^\circ] = 0.5657 \times \sin(-19.49^\circ) = -0.1887 \text{ pu} \end{aligned}$$

$$\begin{aligned} \text{Actual reactive power output of the generator} &= -0.1887 \times 150 \\ &= -28.31 \text{ Mvar or } 28.31 \text{ Mvar flowing towards the transformer} \end{aligned}$$

$$\text{Alternative approach: Use } Q = \frac{V}{X_{tr}} (V_1' \cos \theta_1' - V)$$

where θ_1' is the phasor angle of V_1' :

Note that no further angle adjustment is required since the ref angle of V is at zero degree.

(c) (i) $\delta = 90^\circ$, $E = 0.8974$ pu and $X_s + X_{tr} = 1.51$ pu

$$P_{\max} = \frac{EV}{X_s + X_{tr}} \sin \delta \Big|_{\delta=90^\circ}$$

$$P_{\max} = \frac{0.8974}{1.51} = 0.5943 \text{ pu}$$

$$\text{Actual } P_{\max} = 0.5943 \times 150 = 89.145 \text{ MW}$$

$$I \Big|_{\delta=90^\circ} = \frac{E - V}{j(X_s + X_{tr})} = \left(\frac{0.8974 \angle 90^\circ - 1 \angle 0^\circ}{1.51 \angle 90^\circ} \right) = 0.8898 \angle 48.09^\circ \text{ pu}$$

$$\text{Power factor} = \cos 48.09^\circ = 0.6678 \text{ lead}$$

(c) (ii) $\delta = 90^\circ$, $E' = 1.2 \times 0.8974$ pu and $X_s + X_{tr} = 1.51$ pu

$$P_{\max} = \frac{E'V}{X_s + X_{tr}} \sin \delta \Big|_{\delta=90^\circ}$$

$$P_{\max} = \frac{1.2 \times 0.8974}{1.51} = 0.7132 \text{ pu}$$

$$\text{Actual } P_{\max} = 0.7132 \times 150 = 106.96 \text{ MW}$$

$$I \Big|_{\delta=90^\circ} = \frac{E' - V}{j(X_s + X_{tr})} = \left(\frac{1.2 \times 0.8974 \angle 90^\circ - 1 \angle 0^\circ}{1.51 \angle 90^\circ} \right) = 0.9733 \angle 42.88^\circ \text{ pu}$$

$$\text{Power factor} = \cos 42.88^\circ = 0.7328 \text{ lead}$$